

A smart home project integrates devices to automate lighting, security, and appliances, enhancing convenience and energy efficiency.

SMART HOME

For a better life

- youssef moharm 23101517
 - Yassin ali attia 23101505
 - Wessam yehia 23101877
 - Nour rahsed 23101495
-

1-Rain Detection Alarm Circuit

This project demonstrates a basic rain detection system using a rain sensor, jumper wires, a buzzer, and a 9V battery. The system aims to detect the presence of rain and activate the buzzer as an alert. The rain sensor detects moisture on its surface, sending a signal to a connected circuit, which triggers the buzzer to emit a sound.

Components Used:

Rain Sensor: The primary component used to detect rain or moisture. It typically consists of a sensor pad that reacts to water, completing the circuit when moisture is detected.

Jumper Wires: These are used to connect the rain sensor, buzzer, and power source. They provide the necessary electrical connections to complete the circuit.

Buzzer: The output device that emits sound when the rain sensor detects moisture. It serves as an audible alert for the user.

9V Battery: The power source used to supply energy to the circuit.

Circuit Description

Rain Sensor: The rain sensor consists of a conductive surface that detects moisture. When rain or water makes contact with the sensor's surface, it causes a change in resistance, sending a signal to the circuit. This signal is sent through the jumper wires.

Jumper Wires: The wires are used to connect the rain sensor to the buzzer and the 9V battery. They are placed in such a way that when the rain sensor detects moisture, the signal is relayed to the buzzer, activating it.

Buzzer: The buzzer is connected in such a way that when the rain sensor sends a signal (indicating the presence of rain), it triggers the buzzer to sound, alerting the user.

9V Battery: The 9V battery powers the entire circuit, providing the necessary electrical energy to the rain sensor and buzzer.

Connections on the Breadboard:

1. Power Supply:

1. **Connect the positive terminal of your battery** (or power source) to the **positive rail** of the breadboard.
 2. **Connect the negative terminal of the battery** to the **negative rail** of the breadboard.
-

2. Rain Sensor:

1. Take the two terminals (wires) of the rain sensor:
 - Connect one terminal to the **positive rail**.

3. Buzzer:

1. Connect the negative part of the buzzer to the DO of the rain sensor
 2. Connect the other terminal of the **buzzer** to the **positive rail**.
-

4. Testing the Circuit:

1. Place a few drops of water on the rain sensor.
 - The water creates a conductive path between the sensor's terminals, sending a small current to the **Base (B)** of the transistor.
 - The transistor amplifies this current, allowing a larger current to flow from the **Collector (C)** to the **Emitter (E)**, powering the buzzer.
2. If everything is connected properly, the buzzer will sound when the sensor detects water.

Working Principle

When rain falls on the sensor, the water causes the sensor's conductive material to close the circuit. This completes the connection, which allows current to flow and activates the buzzer. The buzzer then produces a sound, indicating the presence of rain.

Conclusion

This rain detection system is a simple yet effective way to alert users when it starts to rain. It uses basic components such as a rain sensor, jumper wires, a buzzer, and a 9V battery. This type of system can be extended for more advanced applications like automation systems or weather stations.

2-Dark-Activated LED Using LDR and Transistor

Objective:

The goal of this project is to design a light-sensitive circuit that turns on an LED in the absence of light. The circuit uses an LDR (Light Dependent Resistor), BC 547 transistor, and a 100k Ω resistor to detect low light levels and activate the LED when it is dark.

Materials Used:

LED (Light Emitting Diode): The LED emits light when current flows through it. It will turn on when the transistor is activated.

LDR (Light Dependent Resistor): A resistor whose resistance increases when light levels decrease (in darkness). It is used to detect the ambient light levels.

BC 547 Transistor: An NPN transistor that acts as a switch, turning the LED on when activated by the LDR.

100k Ω Resistor: A resistor that limits the current flowing into the base of the transistor, protecting the transistor from excessive current.

9V Battery: The power source that supplies the necessary voltage to the circuit.

Jumper Wires: These wires are used to connect the components together to complete the circuit.

Circuit Description:

LDR (Light Dependent Resistor): The LDR detects light levels. In bright conditions, the resistance of the LDR is low, and in darkness, its resistance becomes high. The LDR is connected in such a way that it controls the base of the BC 547 transistor.

BC 547 Transistor: The BC 547 is an NPN transistor. When the LDR detects darkness (high resistance), it triggers the base of the transistor, allowing current to flow from the collector to the emitter. This action turns the LED on.

100k Ω Resistor: This resistor is connected to the base of the BC 547 transistor to limit the current flowing into the transistor's base, ensuring the transistor operates within safe limits.

LED (Light Emitting Diode): The LED is connected in series with the transistor. When the transistor is switched on, current flows through the LED, causing it to light up.

9V Battery: The battery powers the entire circuit, providing the necessary voltage to the transistor and LED.

Connections on the Breadboard:

1. Power Supply:

1. **Battery positive terminal** → Breadboard positive rail.
 2. **Battery negative terminal** → Breadboard negative rail.
-

2. LDR (Light Dependent Resistor):

1. **Pin 1 of LDR** → Breadboard positive rail.
 2. **Pin 2 of LDR** → Junction point (shared with **Base (B)** of transistor and one leg of the 10 kΩ resistor).
-

3. 10 kΩ Resistor:

1. **One leg of the resistor** → Junction point (shared with **LDR Pin 2** and **Base (B)** of transistor).
 2. **Other leg of the resistor** → Breadboard negative rail.
-

4. NPN Transistor (e.g., BC547):

1. **Base (B)** → Junction point (shared with **LDR Pin 2** and **one leg of the 10 kΩ resistor**).
 2. **Emitter (E)** → Breadboard negative rail.
 3. **Collector (C)** → Cathode (shorter pin) of the LED.
-

5. LED:

1. **Cathode (shorter pin)** → Collector (C) of the transistor.
2. **Anode (longer pin)** → One leg of the 330 Ω resistor.

Working Principle:

Darkness Detection: In low light or darkness, the LDR's resistance increases. This higher resistance at the LDR's output causes a lower current to flow into the base of the BC 547 transistor.

Transistor Switching: When the LDR detects darkness (high resistance), the reduced base current is enough to turn on the transistor. As a result, current flows from the collector to the emitter of the transistor.

LED Activation: Once the transistor is turned on, current flows through the LED, turning it on. The LED lights up in response to the low light conditions.

Bright Light Behavior: In bright light, the LDR's resistance decreases, which prevents sufficient current from reaching the base of the transistor. The transistor remains off, and the LED stays off.

Circuit Diagram:

(Insert a diagram here showing the LDR connected to the base of the BC 547 transistor, the LED connected between the collector and the positive terminal of the battery, and the 100k Ω resistor in series with the LDR and base of the transistor.)

Conclusion:

This project demonstrates how a simple circuit can be used to turn on an LED when it is dark. By using an LDR to detect light levels and a BC 547 transistor to switch the LED on or off, the circuit effectively responds to ambient light conditions. This circuit can be used in applications such as automatic lighting systems or light-sensitive alarms.

3-Traffic Light Circuit

Objective:

The goal of this project is to design a traffic light circuit that simulates the operation of a real - world traffic signal system. The circuit utilizes LEDs to represent the red, yellow, and green lights, along with a 555 timer IC and other components to create timed switching between the lights.

Materials Used:

1. **LEDs (Red, Yellow, Green):** Represent the three traffic light states (Stop, Get Ready, Go).
 2. **555 Timer IC:** A versatile IC used to generate timed signals for switching between LEDs.
 3. **Resistors:** Used to limit the current to LEDs and set the timing interval for the 555 timer.
 4. **Capacitor:** Works with the resistors to control the timing in the circuit.
 5. **9V Battery:** Powers the circuit.
 6. **Jumper Wires:** Used to connect the components on the breadboard.
 7. **Breadboard:** Platform to assemble the circuit without soldering.
-

Circuit Description:

1. **555 Timer IC:**
 - The 555 timer operates in **astable mode**, continuously cycling through ON and OFF states.
 - These states are used to create delays for switching the LEDs.
 2. **LEDs and Resistors:**
 - The red, yellow, and green LEDs are connected to the output of the timer through resistors to protect them from excessive current.
 - Each LED lights up for a set duration to mimic traffic light behavior.
 3. **Capacitor and Resistors (RC Timing):**
 - The capacitor and resistors connected to the timer determine the interval between the switching of LEDs.
-

Connections on the Breadboard:

1. Power Supply:

1. **Battery positive terminal** → Breadboard positive rail.
 2. **Battery negative terminal** → Breadboard negative rail.
-

2. 555 Timer IC Pins:

1. **Pin 1 (GND):** Connect to the **negative rail** of the breadboard.
 2. **Pin 2 (Trigger):** Connect to the junction of the capacitor and resistor in the RC network.
 3. **Pin 3 (Output):** Connect to the resistors and LEDs as described below.
 4. **Pin 4 (Reset):** Connect to the **positive rail** (to keep the timer active).
 5. **Pin 5 (Control Voltage):** Connect to the ground via a **0.01 μ F capacitor** (optional, for stability).
 6. **Pin 6 (Threshold):** Connect to the junction of the capacitor and resistor in the RC network (same as Pin 2).
 7. **Pin 7 (Discharge):** Connect to one end of the timing resistor (used for the RC network).
 8. **Pin 8 (VCC):** Connect to the **positive rail** of the breadboard.
-

3. LEDs (Red, Yellow, Green):

1. **Red LED:**
 - **Cathode (shorter pin):** Connect to Pin 3 (Output) of the 555 timer via a **330 Ω** resistor.
 - **Anode (longer pin):** Connect to the **positive rail**.
2. **Yellow LED:**
 - **Cathode (shorter pin):** Connect to Pin 3 (Output) of the 555 timer via a **330 Ω** resistor.
 - **Anode (longer pin):** Connect to the **positive rail**.
3. **Green LED:**
 - **Cathode (shorter pin):** Connect to Pin 3 (Output) of the 555 timer via a **330 Ω** resistor.

- **Anode (longer pin):** Connect to the **positive rail**.
-

4. Resistors and Capacitor (RC Network):

1. Timing Resistor:

- One leg → Pin 7 (Discharge) of the 555 timer.
- Other leg → Positive rail.

2. Capacitor:

- Positive leg → Junction between **Pin 2 (Trigger)** and **Pin 6 (Threshold)**.
- Negative leg → Negative rail.

Conclusion:

This project demonstrates the implementation of a simple traffic light system using a 555 timer IC. The LEDs represent the real-world operation of traffic signals, switching sequentially based on the timer's output. This circuit can be further enhanced for real-world applications by integrating sensors or microcontrollers.

4-Touch Sensor Circuit

Objective:

The goal of this project is to design a touch-sensitive circuit that activates an LED when a touch is detected. The circuit uses a BC547 transistor, a 10MΩ resistor, and human touch as a triggering mechanism to turn the LED on.

Materials Used:

1. **LED (Light Emitting Diode):** Emits light when current flows through it and turns on upon touch detection.
 2. **BC547 Transistor:** An NPN transistor that acts as a switch, controlling the LED when activated by touch.
 3. **10MΩ Resistor:** Limits the current to the transistor base, ensuring stable operation and avoiding false triggering.
 4. **9V Battery:** Provides the necessary voltage to power the circuit.
 5. **Jumper Wires:** Used to connect all components on the breadboard.
 6. **Breadboard:** A platform to assemble the circuit without soldering.
-

Circuit Description:

1. **Touch Input:**
 - When the user touches the input terminal connected to the base of the BC547 transistor, a small amount of current flows due to the skin's conductivity.
2. **BC547 Transistor:**
 - The small base current amplifies within the transistor, switching it on and allowing current to flow from the collector to the emitter. This action turns the LED on.
3. **10MΩ Resistor:**
 - Connected to the base of the transistor to prevent excessive current flow and avoid unintentional triggering of the circuit.
4. **LED (Light Emitting Diode):**

- Connected to the collector of the transistor. It lights up when the transistor is activated by the touch signal.

Connections on the Breadboard:

1. Power Supply:

- Battery positive terminal → Breadboard positive rail.
- Battery negative terminal → Breadboard negative rail.

2. BC547 Transistor:

- **Base (B):** Connect to one side of the **10M Ω resistor** and the touch input terminal (a bare wire or plate).
- **Collector (C):** Connect to the cathode (shorter pin) of the LED.
- **Emitter (E):** Connect to the breadboard negative rail.

3. 10M Ω Resistor:

- One leg → Base (B) of the BC547 transistor.
- Other leg → Positive rail of the breadboard.

4. LED:

- **Cathode (shorter pin):** Connect to the collector (C) of the transistor.
- **Anode (longer pin):** Connect to the positive rail via a **330 Ω resistor**.

5. 330 Ω Resistor:

- One leg → Anode (long pin) of the LED.
- Other leg → Positive rail.

Working Principle:

1. Touch Detection:

- When the touch terminal is touched, a small current flows into the base of the BC547 transistor due to the human body acting as a weak conductor.

2. Transistor Switching:

- The base current is amplified by the transistor, allowing a larger current to flow from the collector to the emitter.

3. **LED Activation:**

- The amplified current drives the LED, turning it on.

4. **Idle State:**

- In the absence of a touch, no current flows into the base, keeping the transistor off and the LED unlit.

Conclusion:

This project demonstrates the design and working of a simple touch-sensitive circuit. By utilizing the conductivity of human skin and the amplifying property of a BC547 transistor, the circuit effectively detects a touch to activate an LED. This circuit can be applied in touch-based switches, interactive devices, or simple touch-sensitive lighting systems.

5-Gas Sensor Circuit

Objective:

The goal of this project is to design a gas sensor circuit that detects the presence of flammable gas (e.g., methane, LPG) and activates an LED to indicate a gas leak. The circuit uses an MQ-2 gas sensor, BC547 transistor, and a resistor network to detect gas and trigger the LED.

Materials Used:

1. **MQ-5 Gas Sensor:** Detects the presence of flammable gases and outputs a corresponding voltage signal.
 2. **BC547 Transistor:** An NPN transistor that acts as a switch, controlling the LED when the gas sensor detects gas.
 3. **LED (Light Emitting Diode):** Lights up to indicate gas detection.
 4. **10k Ω Resistor:** Limits current to the base of the BC547 transistor, ensuring proper operation.
 5. **1k Ω Resistor:** Limits current through the LED to prevent damage.
 6. **9V Battery:** Provides the necessary voltage to power the circuit.
 7. **Jumper Wires:** Used to connect all components on the breadboard.
 8. **Breadboard:** A platform to assemble the circuit without soldering.
-

Circuit Description:

1. **MQ-5 Gas Sensor:**
 - The MQ-2 gas sensor detects gas and outputs a voltage proportional to the gas concentration. This output voltage is fed to the base of the BC547 transistor.
2. **BC547 Transistor:**
 - The small base current from the gas sensor is amplified within the transistor, switching it
 - on and allowing current to flow from the collector to the emitter. This action turns on the LED.
3. **10k Ω Resistor:**
 - Connected to the base of the BC547 transistor to limit the current from the gas sensor and ensure stable operation.

4. LED (Light Emitting Diode):

- Connected to the collector of the transistor. It lights up when the transistor is activated by the gas sensor signal.

5. 1kΩ Resistor:

- Connected in series with the LED to limit current and protect the LED from overcurrent.

Connections on the Breadboard:

1. Power Supply:

- Battery positive terminal → Breadboard positive rail.
- Battery negative terminal → Breadboard negative rail.

2. MQ-5 Gas Sensor:

- **VCC:** Connect to the positive rail of the breadboard.
- **GND:** Connect to the negative rail of the breadboard.
- **OUT:** Connect to one side of the **10kΩ resistor**.

3. 10kΩ Resistor:

- One leg → Output pin of the MQ-2 gas sensor.
- Other leg → Base (B) of the BC547 transistor.

4. BC547 Transistor:

- **Base (B):** Connect to the junction of the 10kΩ resistor and MQ-2 output.
- **Collector (C):** Connect to the cathode (shorter pin) of the LED.
- **Emitter (E):** Connect to the negative rail of the breadboard.

5. LED:

- **Cathode (shorter pin):** Connect to the collector (C) of the BC547 transistor.
- **Anode (longer pin):** Connect to one side of the **1kΩ resistor**.

6. 1kΩ Resistor:

- One leg → Anode (longer pin) of the LED.
- Other leg → Positive rail.

Working Principle:

1. Gas Detection:

- The MQ-5 sensor detects the presence of flammable gas. If gas is detected, the sensor's output voltage increases.

2. Transistor Switching:

- The increased voltage at the sensor's output is fed to the base of the BC547 transistor. This small current amplifies within the transistor, switching it on and allowing current to flow from the collector to the emitter.

3. LED Activation:

- The amplified current drives the LED, turning it on to indicate gas detection.

4. Idle State:

- In the absence of gas, the MQ-5 sensor's output voltage remains low. The transistor stays off, and the LED remains unlit.

Conclusion:

This project demonstrates the design and working of a gas detection circuit. By using an MQ-2 gas sensor and the amplifying property of a BC547 transistor, the circuit effectively detects flammable gas and activates an LED. This circuit can be applied in gas leak detection systems to enhance safety in homes, industries, and laboratories.

Fire Detection Alarm Circuit

Objective:

To design a simple fire detection system using a photodiode as a flame sensor. The circuit activates an alarm (buzzer or LED) when a fire is detected.

Components:

Photodiode (flame sensor)
BC547 NPN transistor (switch)
100k Ω resistor (sensitivity adjustment)
220 Ω resistor (current limiter for LED)
Red LED (visual alarm)
Buzzer (audible alarm)
9V battery (power supply)
Jumper wires (connections)

Circuit Diagram Description:

The photodiode detects light emitted by flames and converts it into a small voltage.

This voltage is amplified by the BC547 transistor, which acts as a switch.

When light from a flame is detected, the transistor allows current to flow, activating the buzzer and/or LED as an alarm.

Circuit Connections:

Connect one terminal of the photodiode to the positive terminal of the 9V battery.

Connect the other terminal of the photodiode to a 100k Ω resistor.

The junction of the photodiode and resistor is connected to the base of the BC547 transistor.

Connect the collector of the BC547 to:

The positive terminal of the buzzer, or

The LED in series with a 220 Ω resistor.

Connect the emitter of the BC547 to the ground rail.

Finally, connect the 9V battery to power the circuit.

Working Principle:

Under normal conditions (no fire), the photodiode receives minimal light, and the BC547 remains off. The buzzer and LED are inactive.

When a flame is detected, the photodiode generates a voltage that drives the base of the BC547 high.

The BC547 switches on, allowing current to flow through the buzzer and/or LED, activating the alarm.

Applications:

This circuit can be used in:

Fire alarm systems for homes or small spaces
Flame detection in industrial setups
Basic safety devices for schools or hobby projects

